

SE Sem IV (R-2019 C scheme) "Mechanical" Dec' 2023

3 Hours [Max Marks: 80]

3 Hours

[Max Marks: 80]

N.B. : (1) Question No 1 is Compulsory.
(2) Attempt any three questions out of the remaining five.
(3) All questions carry equal marks.
(4) Assume suitable data, if required and state it clearly.

Attempt any FOUR

[20]

1 Draw and explain IC 555 as Monostable Multivibrator.

Explain the High pass active filter.

b) Explain various features of logic family.

c. Explain various features of SCR.

d. Explain commutation and suggest with circuit diagram any natural commutation method of SCR.

Compare De multiplexer and Multiplexer.

2. a Explain an ac to DC controlled converter supplying resistive load. Derive an expression for calculating output dc voltage.

[10]

expression for calculating output dc voltage.

b) Describe instrumentation amplifier with labeled diagram. State its application area.

[10]

3 a Explain the necessity of closed loop speed control in DC motor.

[10]

- Explain the necessity of closed loop speed control.
- Draw Differentiator, integrator circuit with output voltage equation.

[10]

4 a Explain need of digital to analogue conversion. How the ADC in MSP430 works?

[10]

b Explain three phase inverter operation with waveforms.

[10]

5 a Draw and explain important sections of MSP 430 microcontroller.

[10]

- Draw and explain important sections of MSP 430 microcontroller.
- Compare digital circuits with Analog circuit. List Application of Each of them.

[10]

6 a Describe speed torque characteristics of DC and AC motors.

[10]

b Compare microprocessor and microcontroller.

[10]