

Marks: 80

- N.B. : (1) Question No 1 is Compulsory.
(2) Attempt any three questions out of the remaining five.
(3) All questions carry equal marks.
(4) Assume suitable data, if required and state it clearly.

1 Attempt any FOUR

[20]

- a Convert the following number systems.

- 1) $(37.31)_{10}$ to Binary
- 2) $(10)_{10}$ to BCD
- 3) $(436.71)_8$ into Hexadecimal

- b Draw and explain 4-bit Carry Look Ahead Adder.

- c With a neat diagram, explain the working of IC7490 Decade Counter.

- d Distinguish between PLA and PAL devices.

- e Write a code in Verilog HDL to implement half adder circuit.

- 2 a A function is defined as $F(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 10, 11, 13, 14, 15)$. Design using single IC 74151. [10]

- b Explain the working of IC7485 with the help of a function table. Draw a neat diagram of an 8-bit comparator using two IC7485. [10]

- 3 a With a neat block diagram, explain the working of 74138 Decoder IC. Design 4:16 decoder using two 74138 ICs. [10]

- b With a neat diagram, explain the working of IC74194. Design it as a Ring Counter. [10]

- 4 a Design a Non-Overlapping Mealy Sequence Detector for sequence 1101. [10]

- b With suitable examples, explain Weighted Codes and Hamming codes. [10]

- 5 a Write a short note on CPLD Devices. How are they different from FPGA Devices? [10]

- b Draw the circuits of NAND and NOR Gates using CMOS devices. Explain the working of each. [10]

- 6 a Write a code in Verilog HDL to implement 4-bit Up-down counter. [10]

- b Design IC74163 to count from binary equivalents of 4 to 15. [10]
