

Sem III (DSE) "R-2019 C Scheme" "ECS", Jan 2023

Time: 3 Hours

Max. Marks: 80 Marks

Solve any Four out of Five

(05 Marks Each)

State & explain the Shockley's current equation of the P-N junction diode.

For the circuit shown below in Fig. 1 draw output waveform if an input signal of 20 V peak-to-peak is applied.

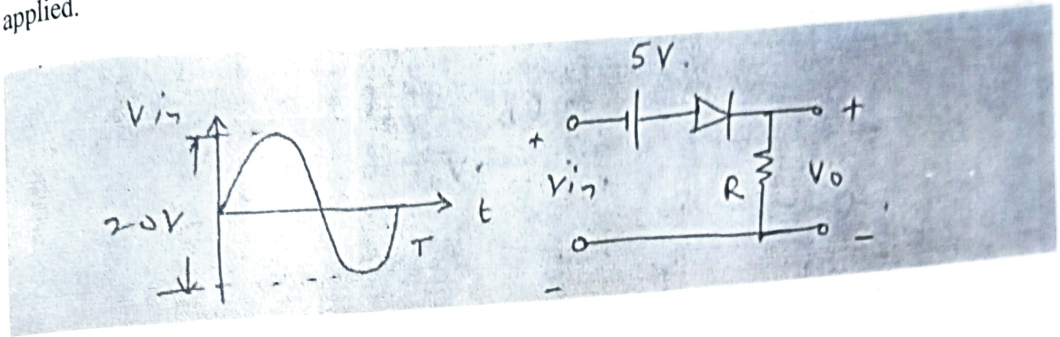


Fig. 1 for Q.2 (B)

- (a) Explain the working principle & operation of solar cell with a neat sketch. 10
- (b) Sketch & explain with appropriate waveforms the capacitor (C) filter. 10
- (c) Draw the circuit diagram & explain the operation of full wave bridge rectifier. 10
2. (a) With neat sketch, describe structure, construction, operation & V-I characteristics of the Schottky diode. 10
- (b) For (any) full wave rectifier, define 'ripple factor' & derive expression for ripple factor (γ). 10
3. (a) With neat sketch, describe the operation of center-tapped full-wave rectifier with appropriate waveforms. 10
- (b) Explain the V-I characteristics of a photo diode with a neat sketch. What is meant by 'dark current'? 10
4. (a) Discuss the working of Zener diode as voltage regulator for changing input supply voltage & changing load resistance. 10
- (b) For (any) full wave rectifier, define 'ripple factor' & derive expression for ripple factor (γ). 10
5. (a) Systematically compare all filter circuits (C, L, L-C & C-L-C) on any five points. 10
- (b) For a light emitting diode, sketch & explain constructional details & discuss the operation. 10
6. (a) With neat sketch, explain the operation of n-channel enhancement MOSFET. 10
- (b) Explain input & output characteristics of BJT in common emitter (CE) configuration. 10
